

DTU



02226 – Networked Embedded Systems

Week 3: MCU Input/Output

Xenofon (Fontas) Fafoutis



Associate Professor

xefa@dtu.dk

www.compute.dtu.dk/~xefa


Digital Logic

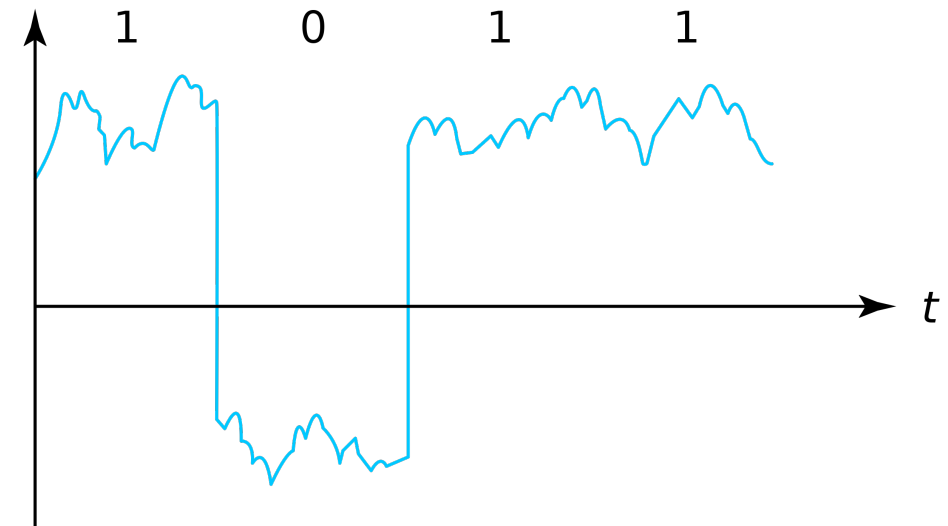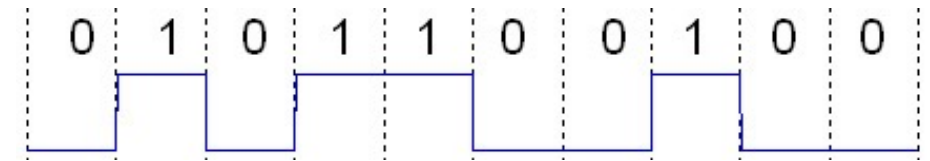- Two distinguishable voltage levels are mapped in two a binary digit
- **High voltage** (typically, the supply voltage) is '1'
- **Low voltage** (typically, the ground) is '0'
- Real world is noisy, but noise can be tolerated
 - E.g. if $V > V_S/2$, then '1'





General Purpose Input/Output (GPIO)

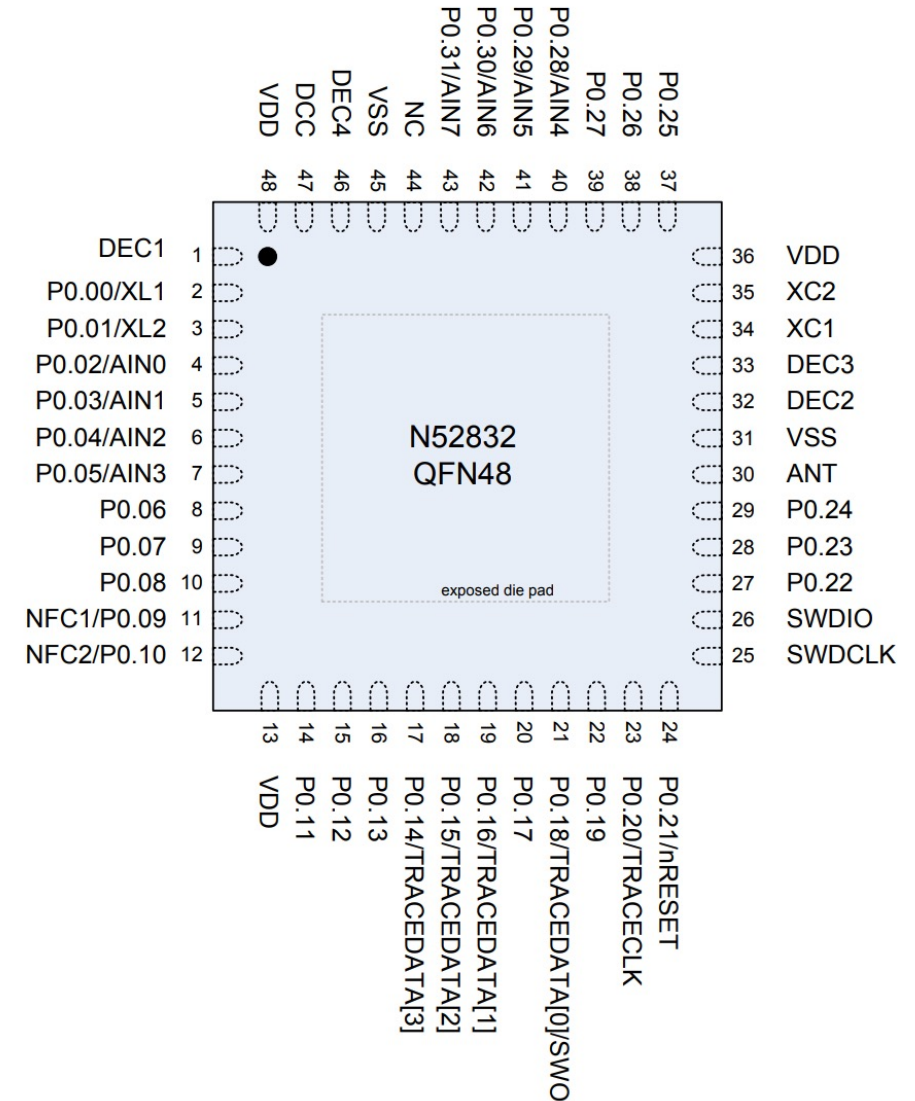- A GPIO is controllable by software and can:
 - Set the logic level of a line to high or '1'
 - Set the logic level of a line to low or '0'
 - Read the logic level of the line
- Example: the nRF2832 has 32 GPIOs
 - Labelled as P0.00-P0.31 in the figure




GPIO Output: Push-Pull Mode

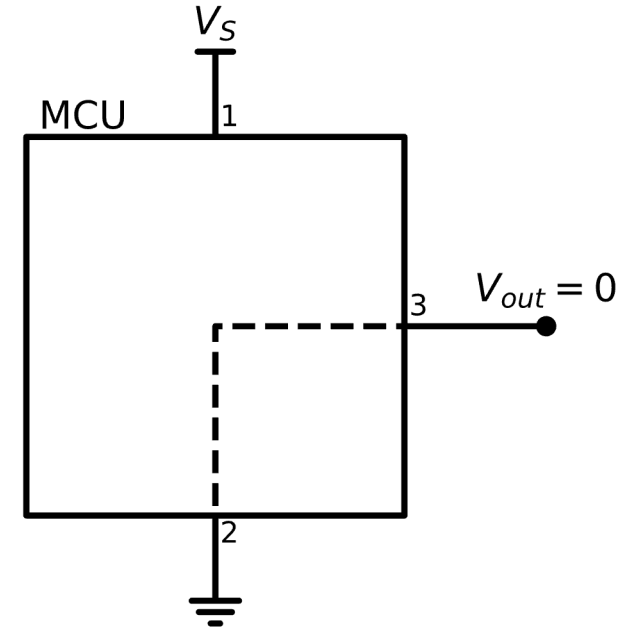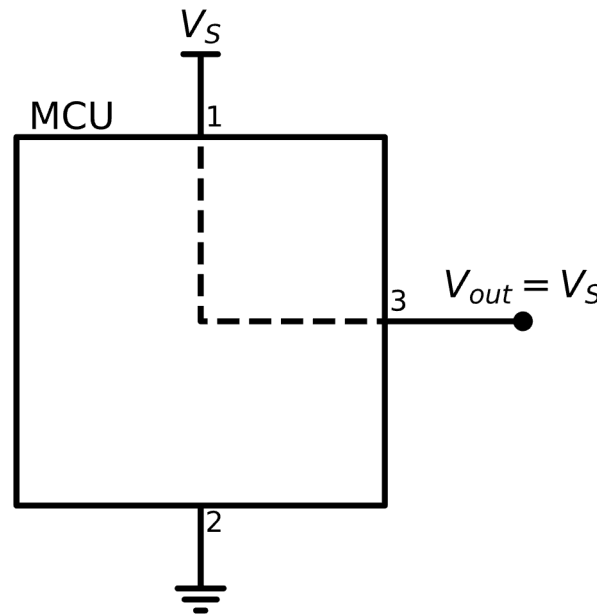- The MCU **drives** the output by actively connecting it to the supply voltage or ground
- When the output voltage is high, the MCU **pushes** the output to V_S
- When the output voltage is low, the MCU **pulls** the output to the ground
- Often push-pull mode is the default output state of the GPIO
- Controlled in **software**




GPIO Output: Push-Pull Mode

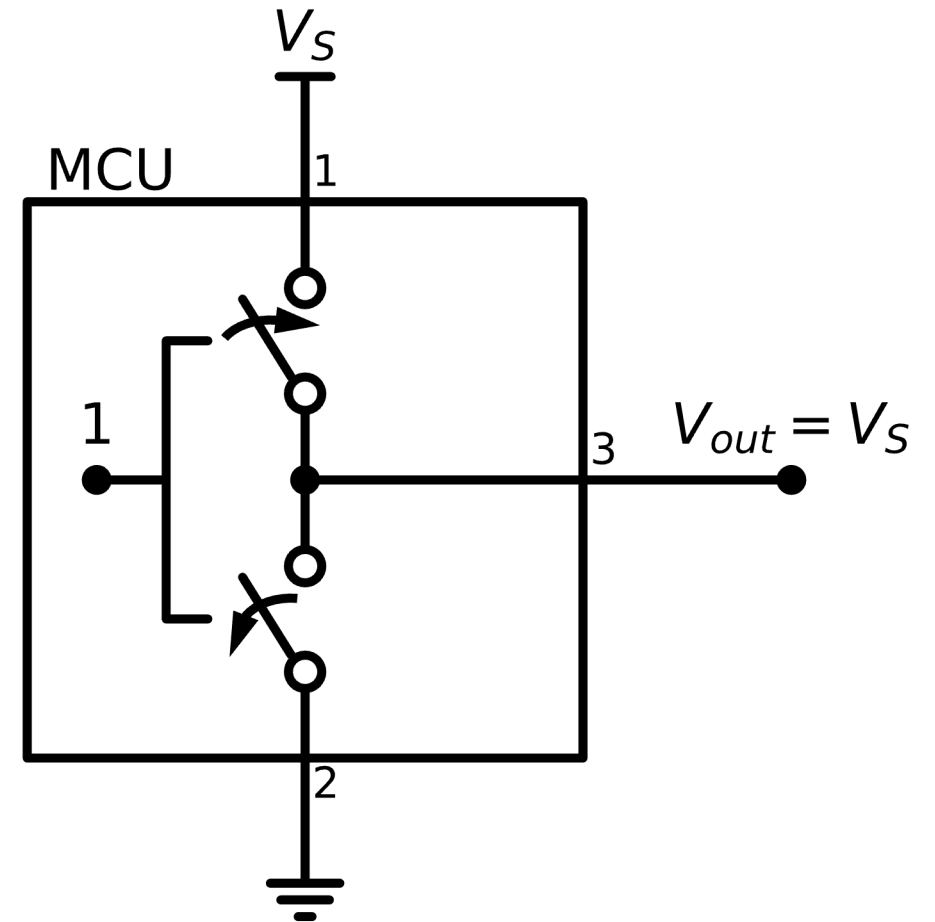- Implemented with MOSFET switches
- Input '1' connects output pin to V_S while simultaneously disconnects it from the ground





GPIO as a Current Source

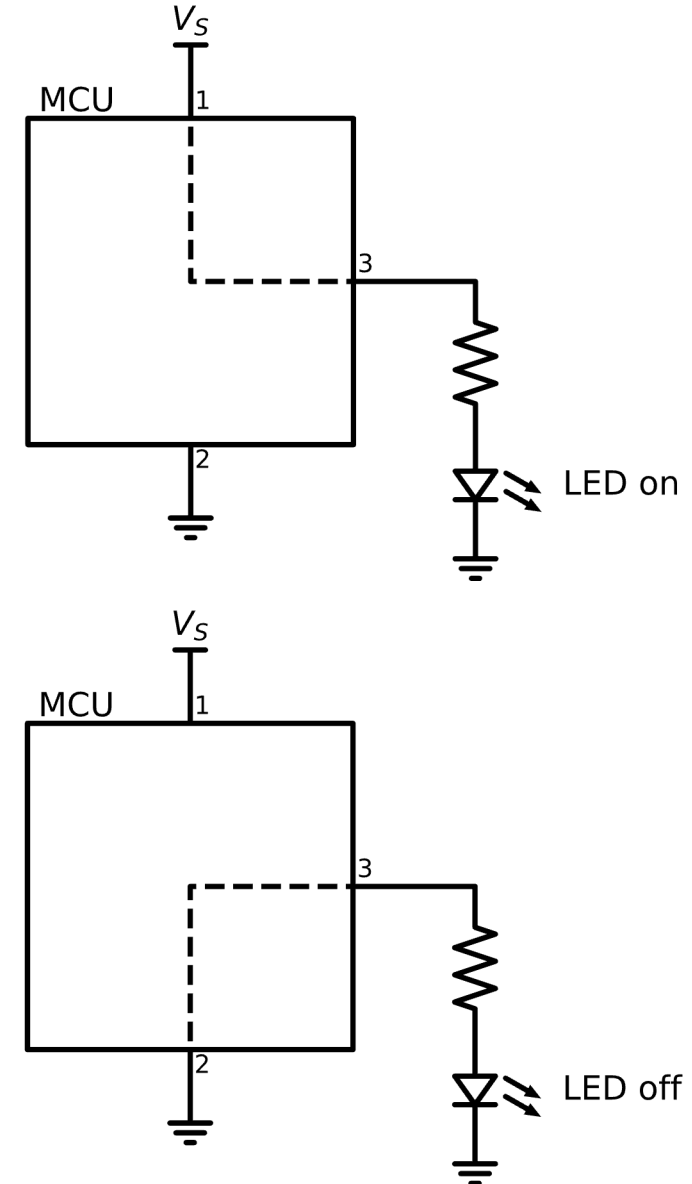- Communication signals are low current signals
- GPIOs can also **source current** to power external components
- MCU can use GPIO as an **on/off switch**
- However, the **output current** of a GPIO is limited (typically, 2-12mA)
- MCU might have some **high drive** GPIOs that can output more current (e.g. 40mA)
- High-power components need to be connected directly to the power source




GPIO as a Current Sink

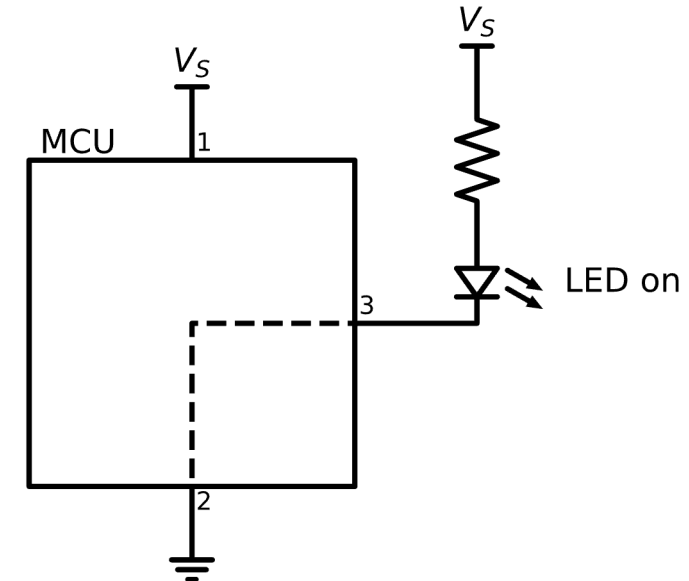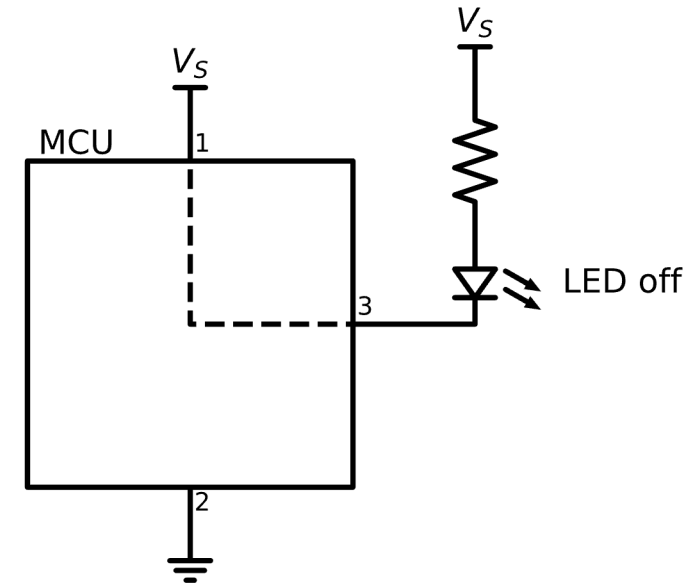- GPIO can also **sink current**
- Current flows inwards
- Closes the circuit by connecting it to the ground
- Logic is reversed
 - '1' turns off the LED
 - '0' turns on the LED
- Sink current also limited




Two MCUs

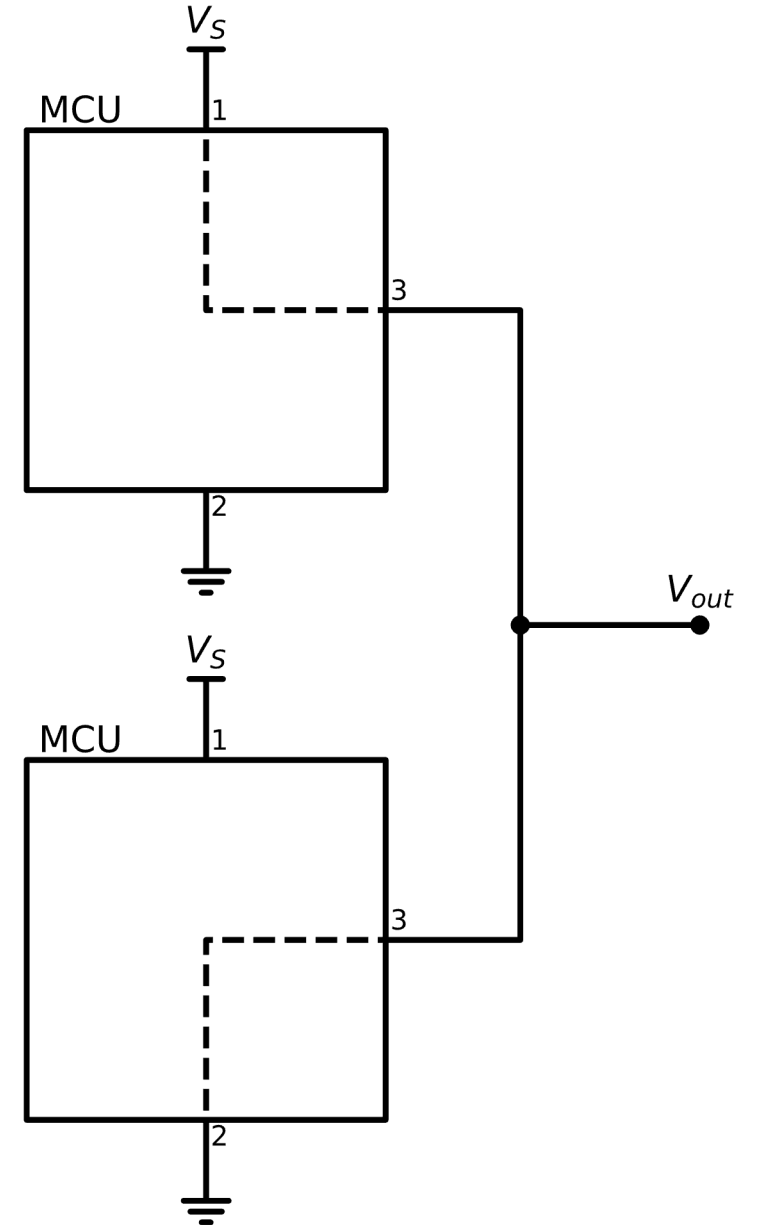- Multiple devices may share the same output line
- What happens if two MCUs drive the same output line?




Two MCUs

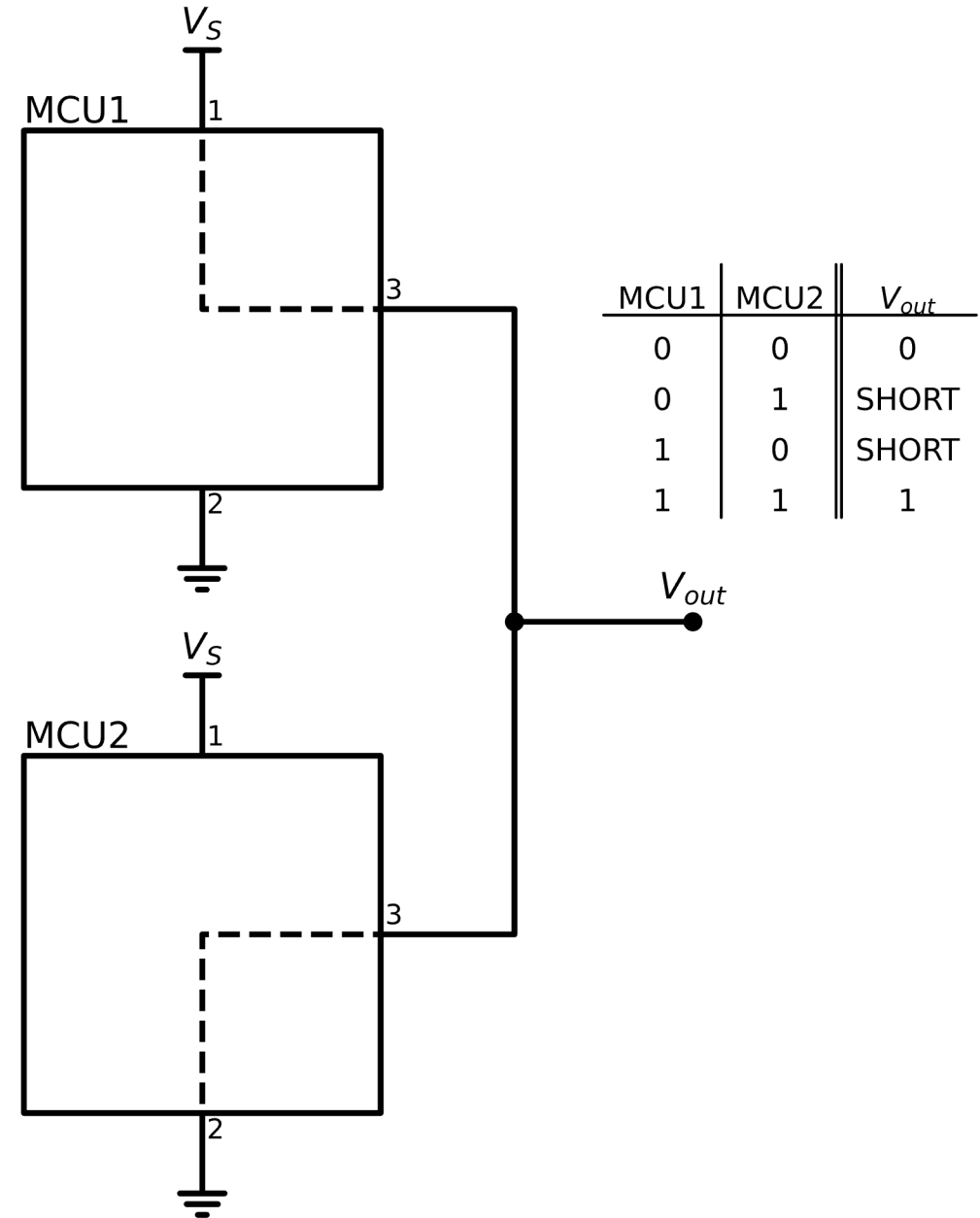- Multiple devices may share the same output line
- What happens if two MCUs drive the same output line?
- If one device pushes the output high while the other pulls it low, we have a **short circuit**
- In general, **only one** device should drive a line
- Two output states are not enough, we need to have the option to **disconnect** the output




Tri-State Logic

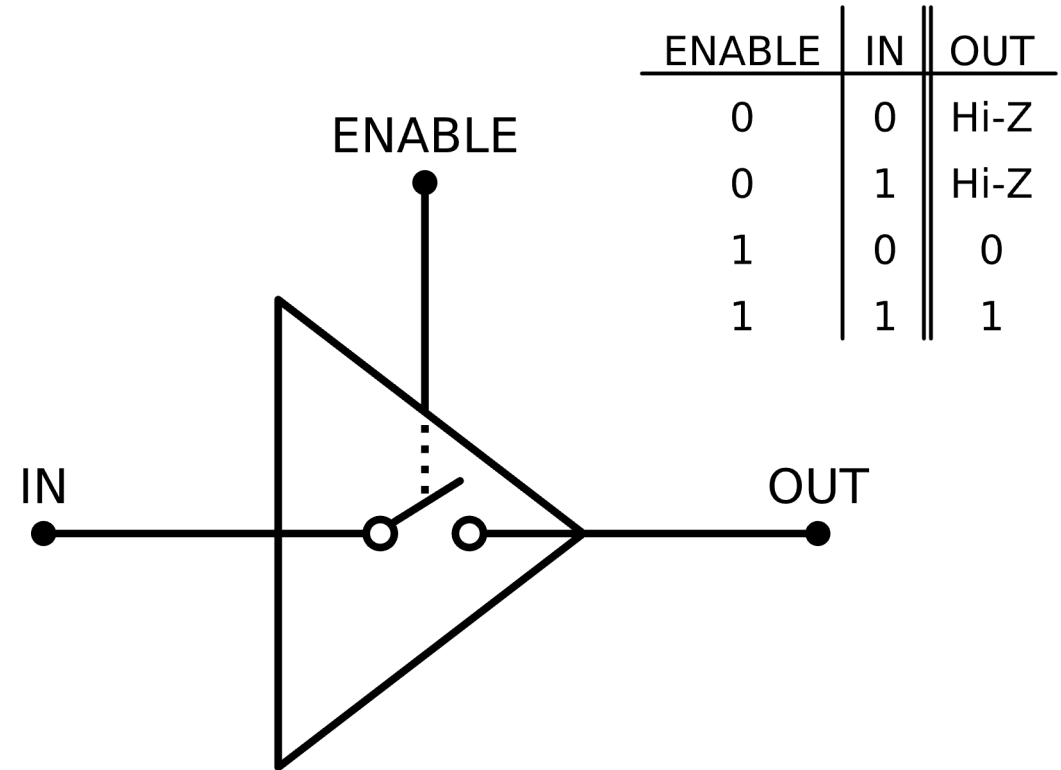- Three States
 - Logical '0' (i.e. low voltage)
 - Logical '1' (i.e. high voltage)
 - High Impedance or Hi-Z (disconnected)
- Tri-state Buffer
 - Implemented with MOSFET switches
 - At open state the resistance is so high that no current can go through
 - Equivalent to open circuit




GPIO Output States

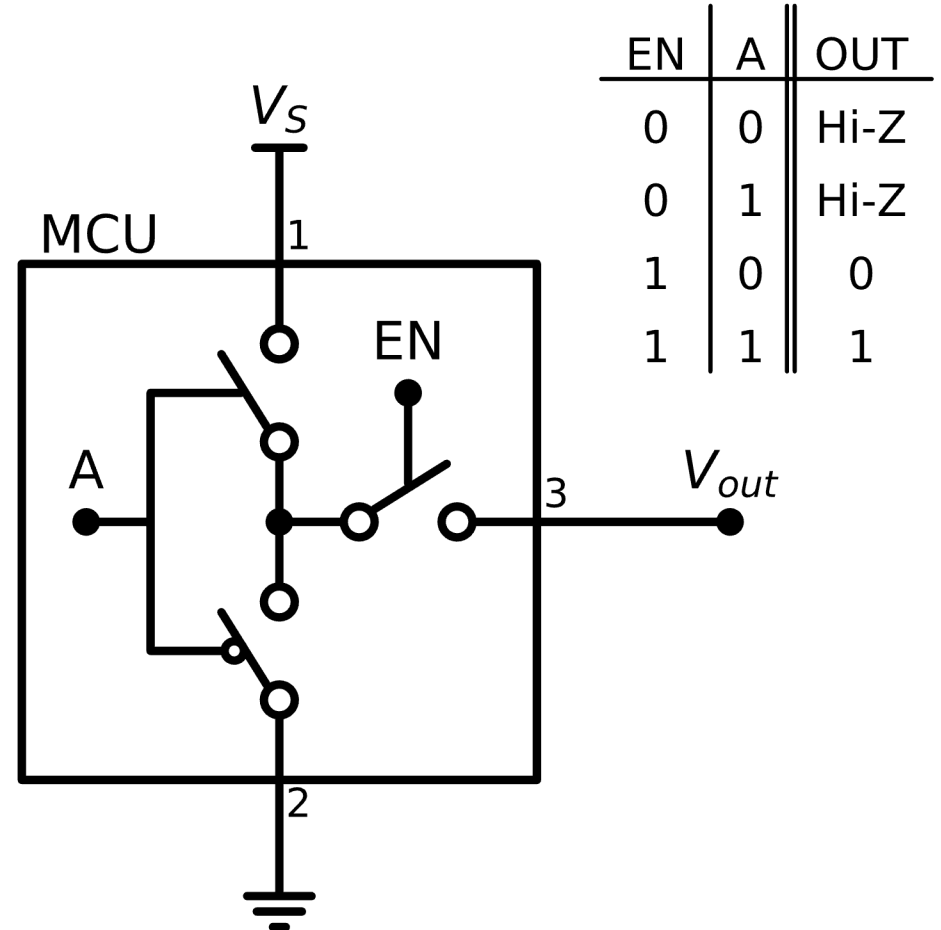- With two controls:
 - Output value (A)
 - Enable (EN)
- GPIO can be:
 - Actively pushed to '1'
 - Actively pulled to '0'
 - Disabled (Hi-Z)




GPIO Input and Input Hysteresis

- **Comparator** is a component that compares two (analogue) input signals and outputs '0' or '1' depending which is larger
- A GPIO input can be implemented by comparing the input signal to $V_S/2$
- Noise close to the threshold creates quick changes between '0' and '1'
- **Input Hysteresis** mitigates this problem by applying two different thresholds
 - To go from '0' to '1', $V > (V_S/2) + V_H$
 - To go from '1' to '0', $V < (V_S/2) - V_H$

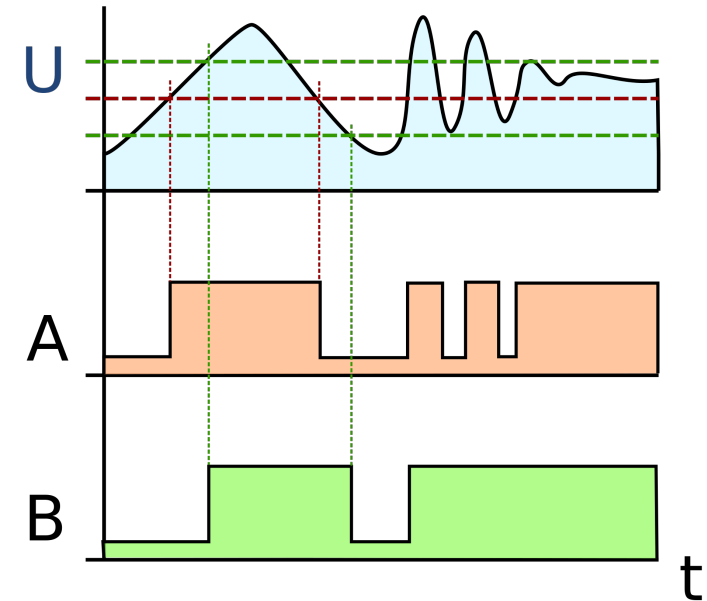


GPIO Input Mode

- When $EN=1$, the input IN equals A

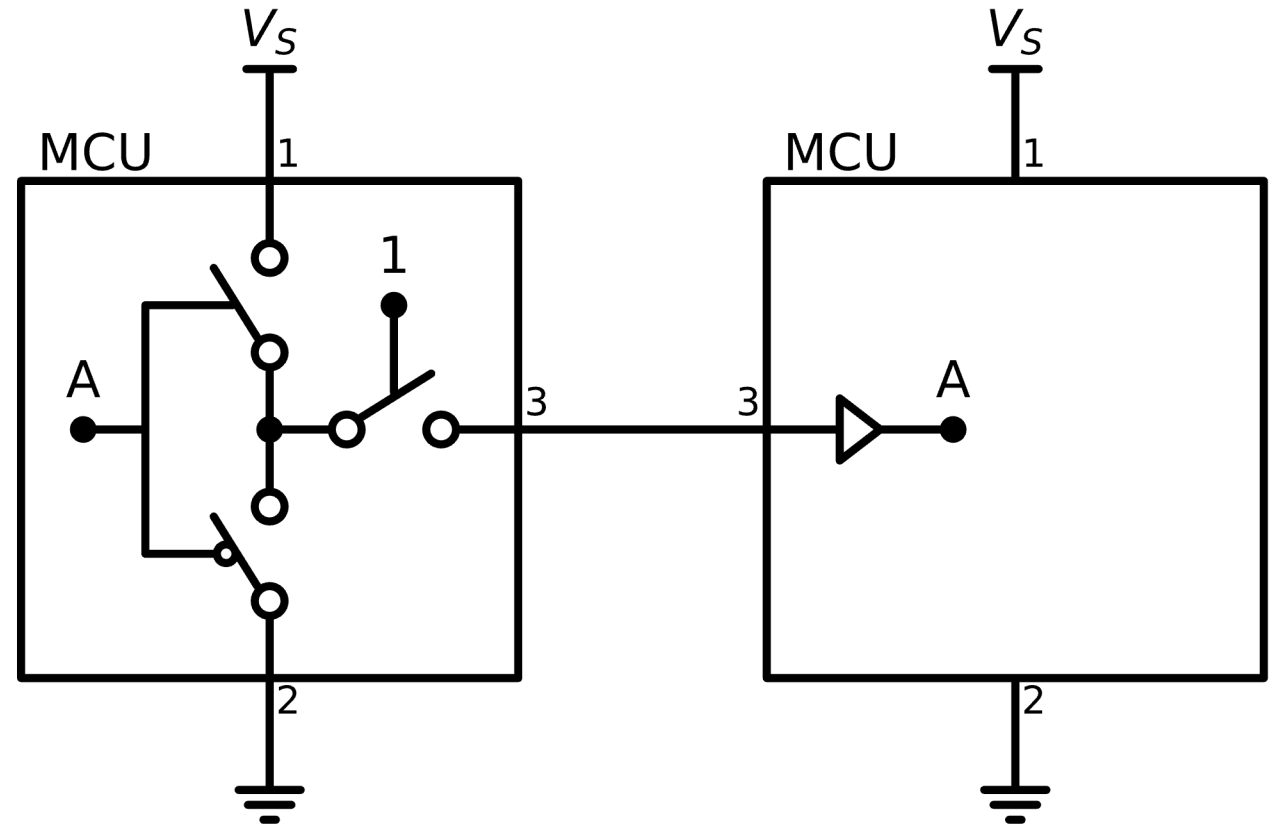


Hardwired Input

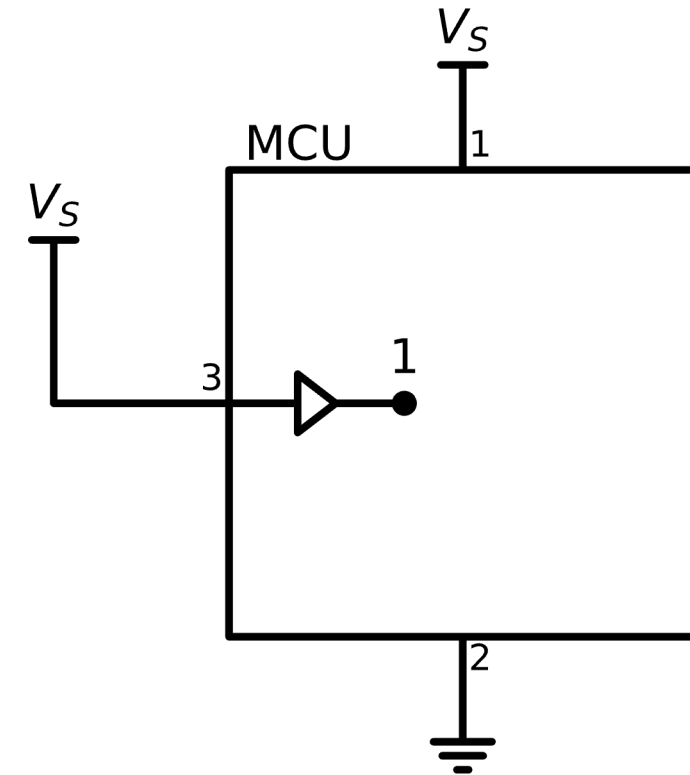- Input can also be hardwired
 - Fixed to have **constant value** in the circuit
- Permanent configuration
 - Assuming input controls some configuration
- As a form of ID
 - Consider a circuit with two MCUs running the same software, but one has Pin3 hardwired to '0' and the other has Pin3 hardwired to '1'
 - Reading Pin3 is a form of self-identification




Reading a Hi-Z output

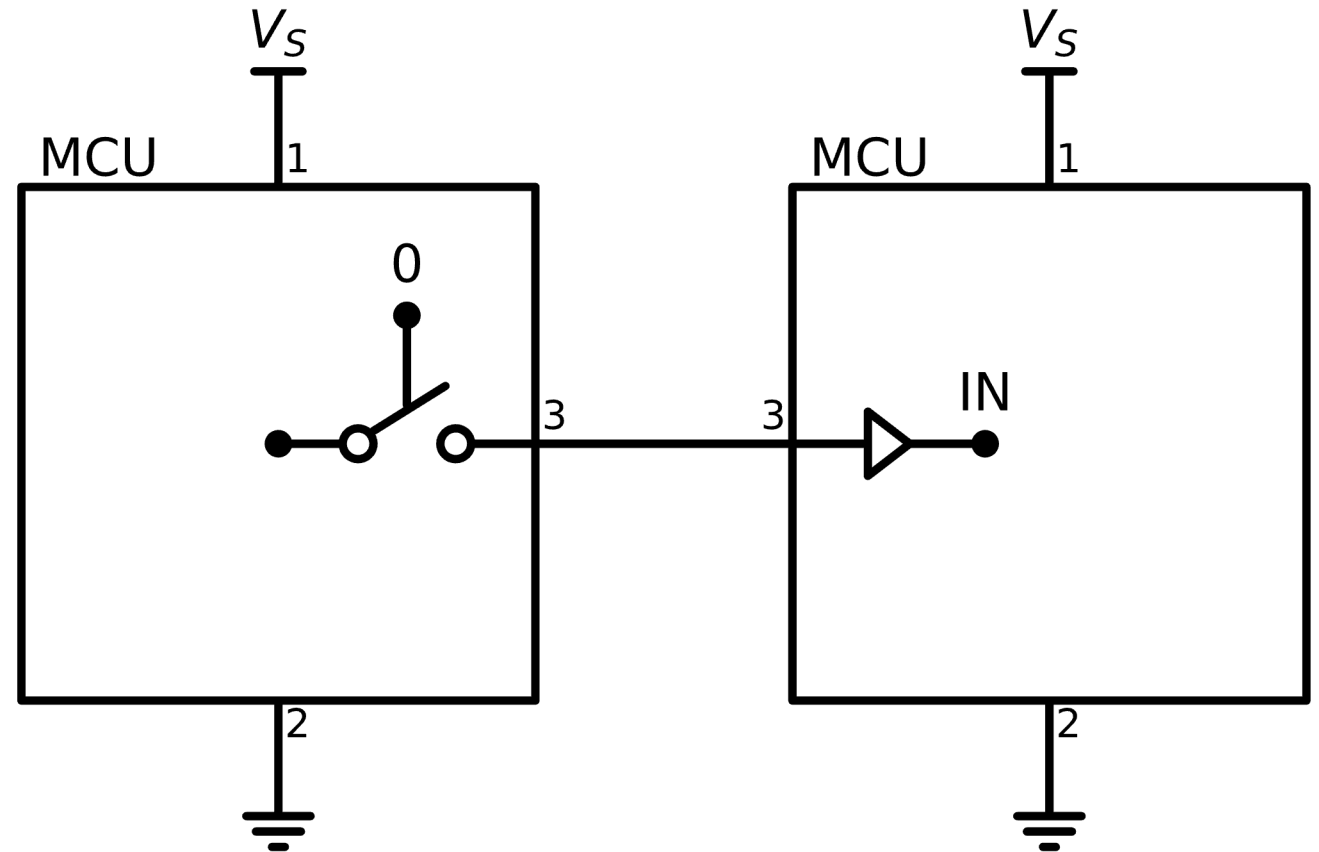- What value will we get if we try to read a disabled output?




Reading a Hi-Z output

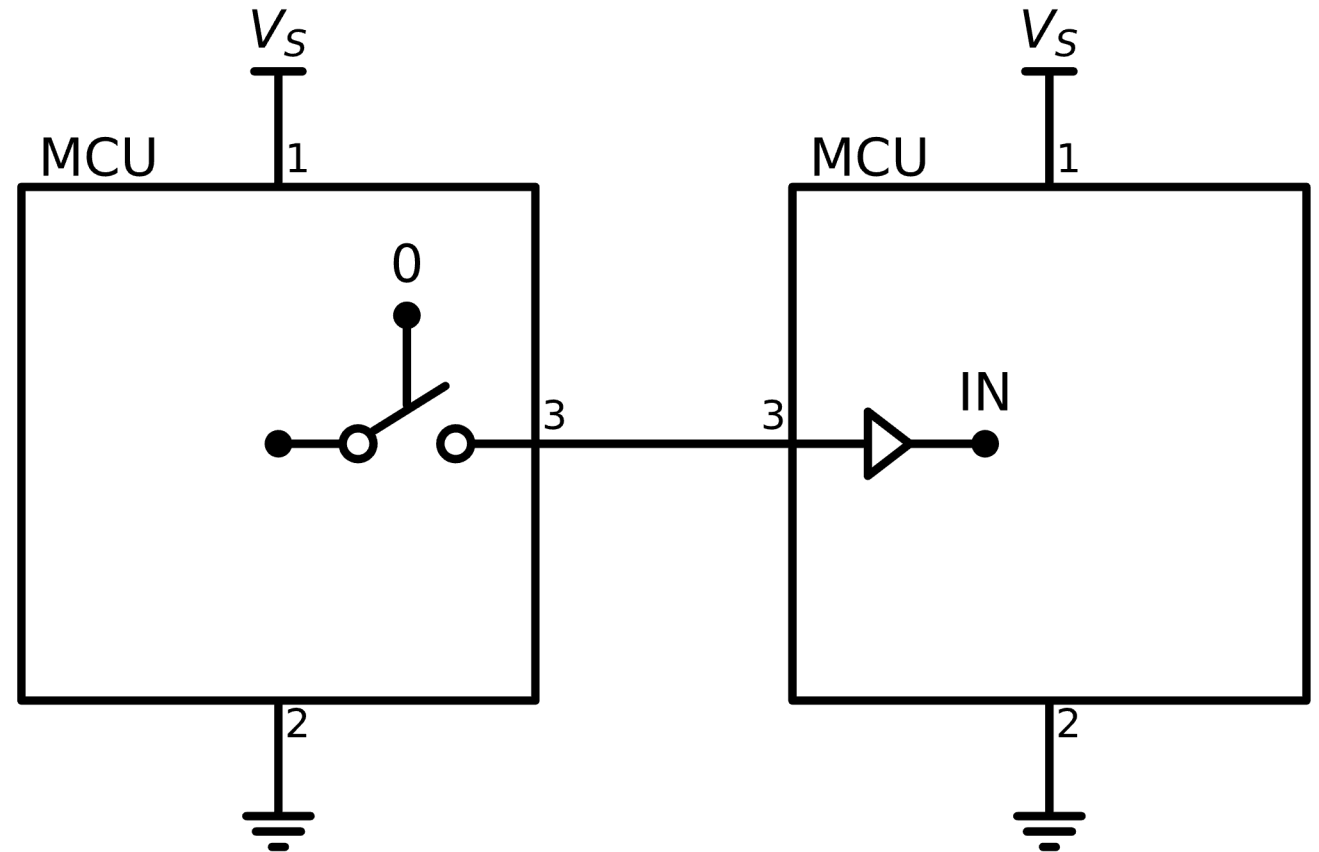- What value will we get if we try to read a disabled output?
- The input is undefined
 - It can be 0 or 1 or can switch between them
- It essentially acts as a tiny antenna, capturing noise from its surroundings
- A Hi-Z pin is **floating**




Pullup and Pulldown Resistors

- They provide **a default state**
- If nobody actively drives the line
 - The pullup resistor will raise the line to '1'
- If the line is actively pulled to '1'
 - No voltage difference across the pullup resistor (no current), line is '1'
- If the line is actively pushed to '0'
 - There is voltage difference across the pullup resistor (current goes through), line is '0'
- Similarly, the pulldown resistor defaults to '0'
- MCU typically supply internal pullup/pulldown resistors

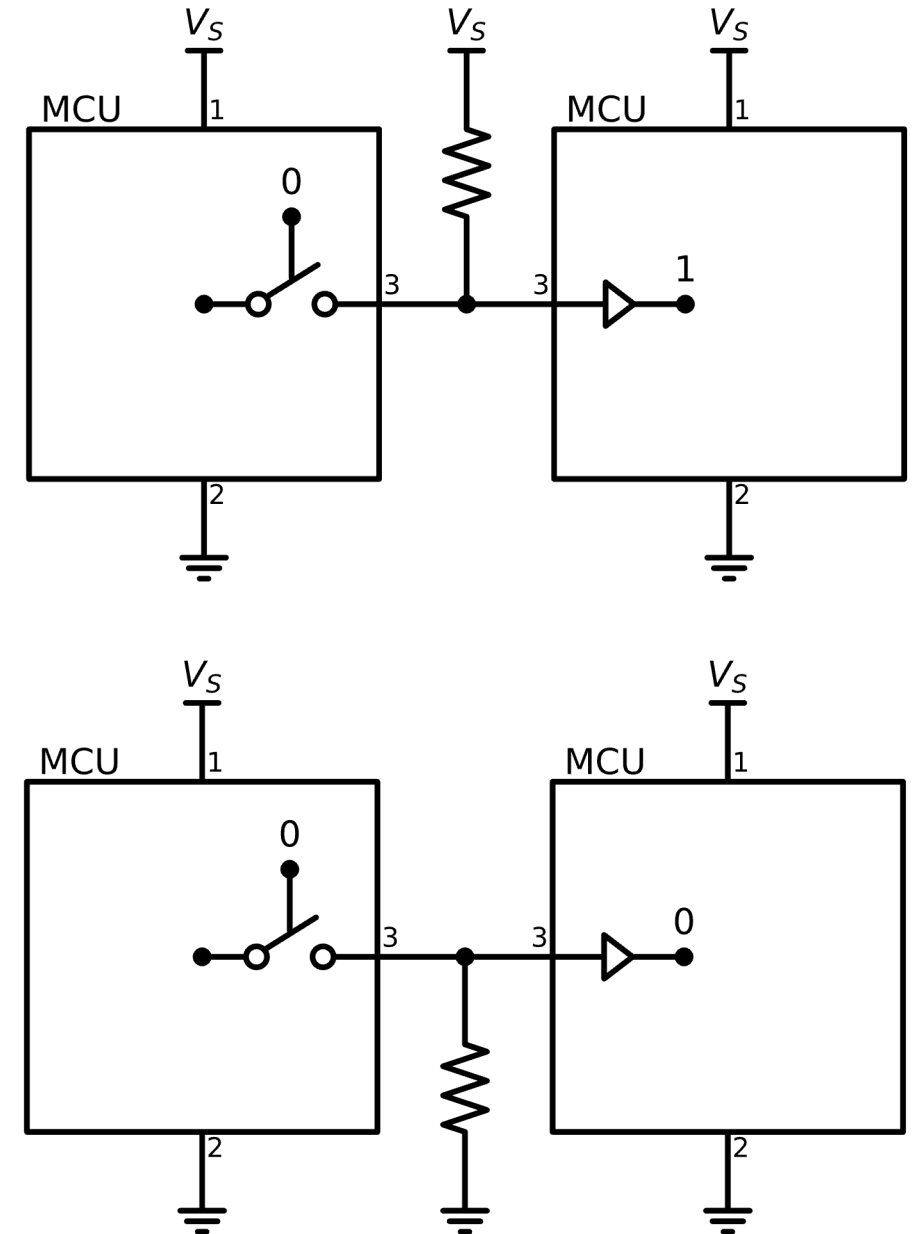

GPIO Output with Pullup

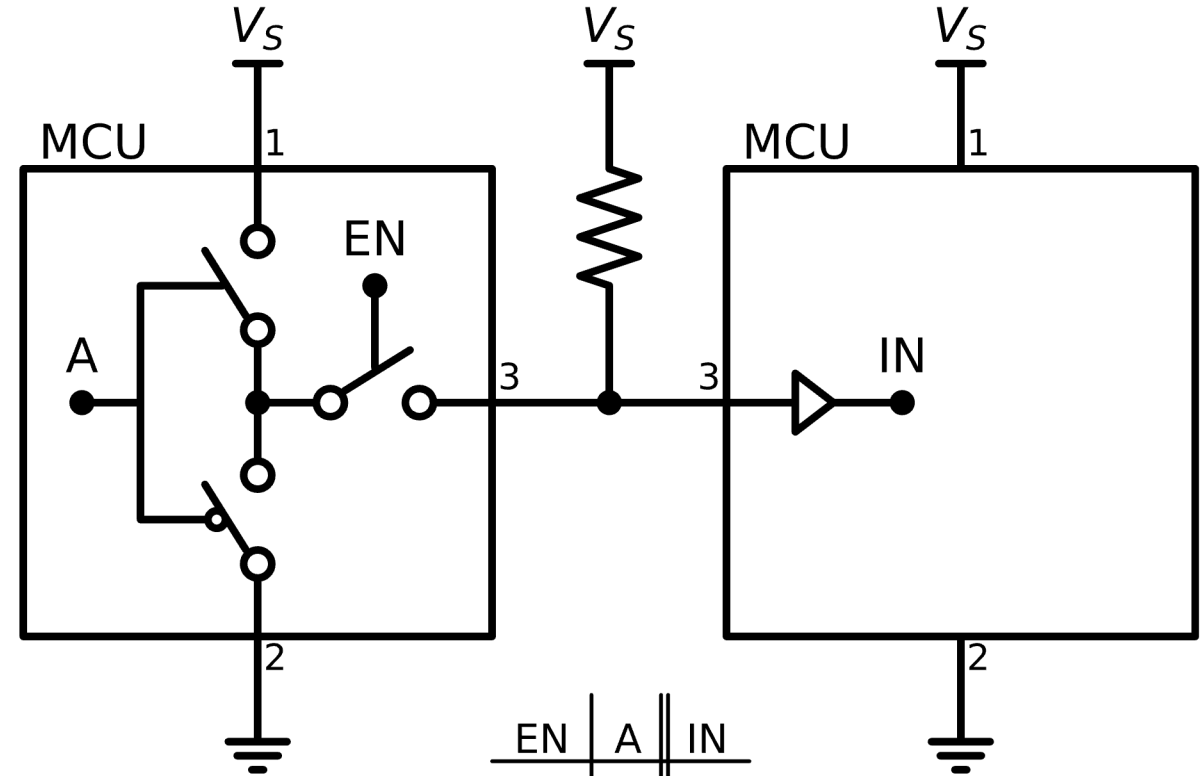
- If output is disabled ($EN='0'$)
 - Pullup resistor determines the input ($IN='1'$)
- If output is enabled ($EN='1'$)
 - Output determines the input ($IN=A$)



EN	A	IN
0	0	1
0	1	1
1	0	0
1	1	1

Multiple MCUs

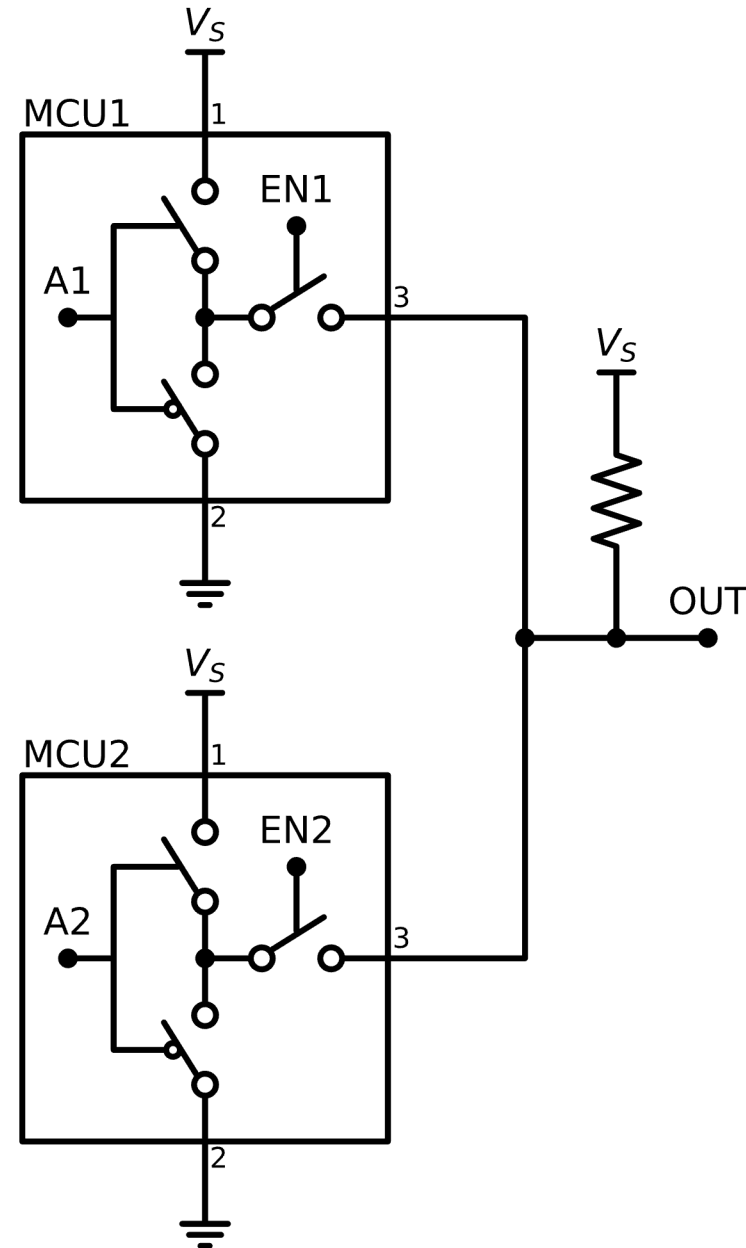
- OK if one output is enabled at a time
- Short circuits are still possible with push-pull outputs
- Is this safe enough?



A1	EN1	A2	EN2	OUT
0	0	0	0	1 (pullup)
0	0	0	1	0 (MCU2)
0	0	1	0	1 (pullup)
0	0	1	1	1 (MCU2)
0	1	0	0	0 (MCU1)
0	1	0	1	0 (both)
0	1	1	0	0 (MCU1)
0	1	1	1	SHORT
1	0	0	0	1 (pullup)
1	0	0	1	0 (MCU2)
1	0	1	0	1 (pullup)
1	0	1	1	1 (MCU2)
1	1	0	0	1 (MCU1)
1	1	0	1	SHORT
1	1	1	0	1 (MCU1)
1	1	1	1	1 (both)

GPIO Output: Open-Drive Mode

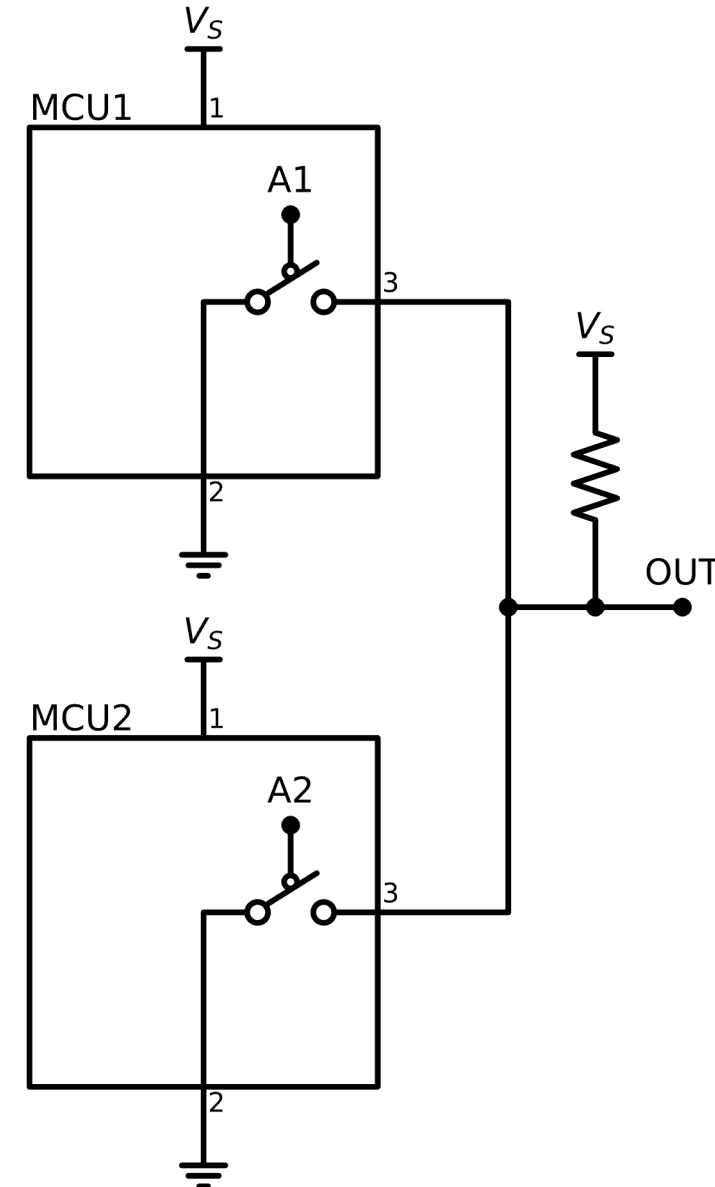
- Open-Drive mode has two states:
 - Logical '0' (i.e. low voltage)
 - Hi-Z (i.e. disconnected)
- Sets the line to '0' **actively**
- Sets the line to '1' **indirectly** by disconnecting the output and letting the pullup resistor raise it to '1'
- The pullup resistor can also be internal
- Open-Drive is used when multiple devices share the same line (safe from shorts)



A1	A2	OUT
0	0	0 (both)
0	1	0 (MCU1)
1	0	0 (MCU2)
1	1	1 (pullup)

Analog-to-Digital Converter (ADC)

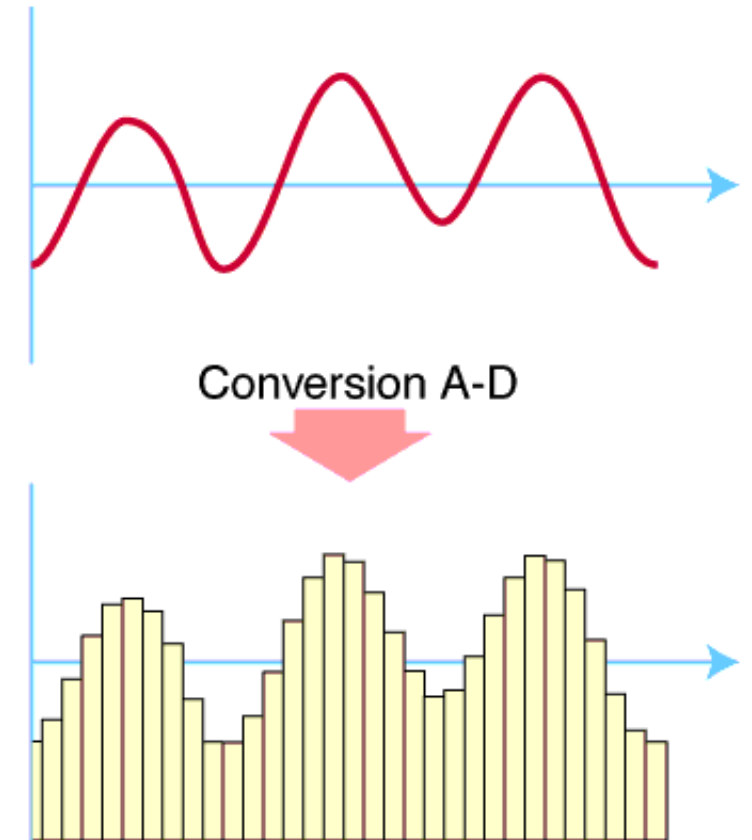- An ADC converts an analogue signal (voltage signal) into a digital signal (series of numbers)
- An ADC essentially measures the voltage of the input and maps it to a number
- The Bit Resolution (M) defines the number of discrete values the ADC can produce
- E.g.: A 12-bit ADC maps the input to a number in $[0, 4095]$, i.e., 2^{12} values



Single-Ended ADC

- Measures input voltage (V_{in}) referenced to the ground
 - Input and ADC have common ground
- The reference voltage (V_{ref}) defines the maximum value that can be measured
 - V_{ref} can be equal to the supply voltage or less
 - Voltages in $[0, V_{ref}]$ are linearly mapped in $[0, 2^M-1]$
 - If $V_{in} > V_{ref}$, $DOUT=2^M$ (saturation)
- Examples:
 - A 12-bit ADC with $V_{ref}=5V$ will map:
 - $V_{in}=0V$ to 0
 - $V_{in}=2.5V$ to 2048
 - $V_{in}=5V$ to 4095
 - $V_{in}=6V$ to 4095



$$DOUT = \frac{V_{in}}{V_{ref}} \cdot 2^M$$

Single-Ended ADC



- Quantisation error
 - The continuous analogue values are mapped to the closest integer
 - The reference voltage (V_{ref}) together with the bit resolution (M) define the voltage resolution (Q)
 - In other words, measurements are in steps or quanta of $Q = V_{ref} / 2^M$
- Examples:
 - A 12-bit ADC with $V_{ref}=5$ V, $Q= 1.22$ mV
 - A 12-bit ADC with $V_{ref}=2.5$ V, $Q= 0.6$ mV
 - A 8-bit ADC with $V_{ref}=5$ V, $Q= 19.5$ mV
 - A 8-bit ADC with $V_{ref}=2.5$ V, $Q= 9.7$ mV
- Trade-off: range vs resolution



$$DOUT = \frac{V_{in}}{V_{ref}} \cdot 2^M$$

ADC: Range vs Resolution



- Assuming an 8-bit ADC and supply voltage 5V
- If I want to measure a signal in [0, 5] Volts
 - I can do it with a 19.5 mV resolution
- If I want to measure a smaller signal in [0,1] Volts with more subtle variations
 - With $V_{ref}=5V$, 19.5 mV resolution may not be enough and DOUT values [52,255] will never be used!
 - Instead with $V_{ref}=1V$, I have 3.9 mV resolution and I use all DOUT values [0,255]

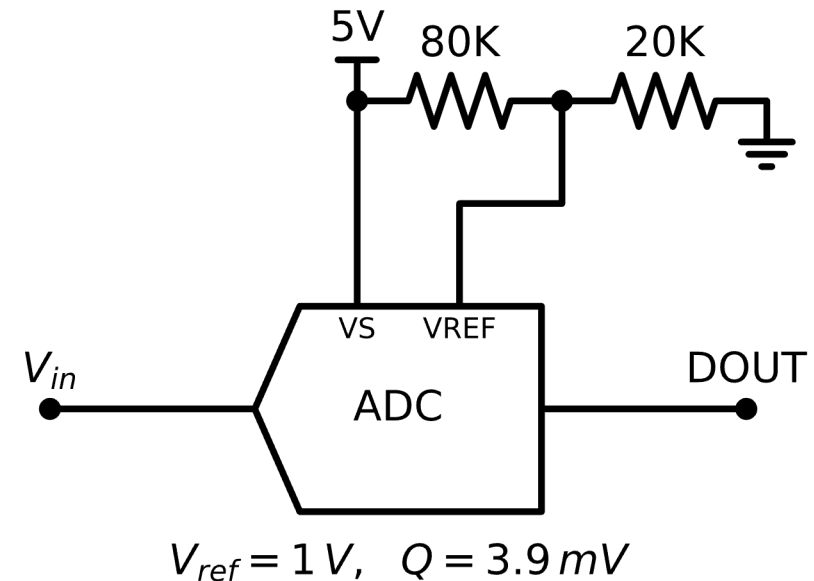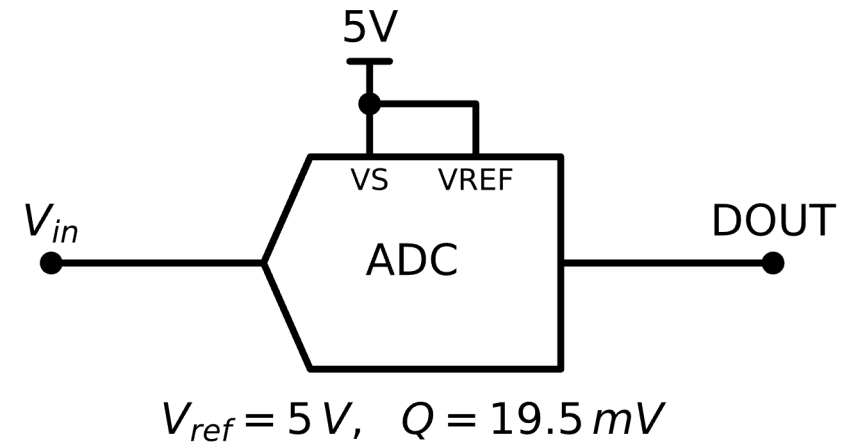

ADC: Range vs Resolution

- Assuming an 8-bit ADC and supply voltage 5V
- If I want to measure a signal in [0, 5] Volts
 - I can do it with a 19.5 mV resolution
- If I want to measure a smaller signal in [0,1] Volts with more subtle variations
 - With $V_{ref}=5V$, 19.5 mV resolution may not be enough and DOUT values [52,255] will never be used!
 - Instead with $V_{ref}=1V$, I have 3.9 mV resolution and I use all DOUT values [0,255]

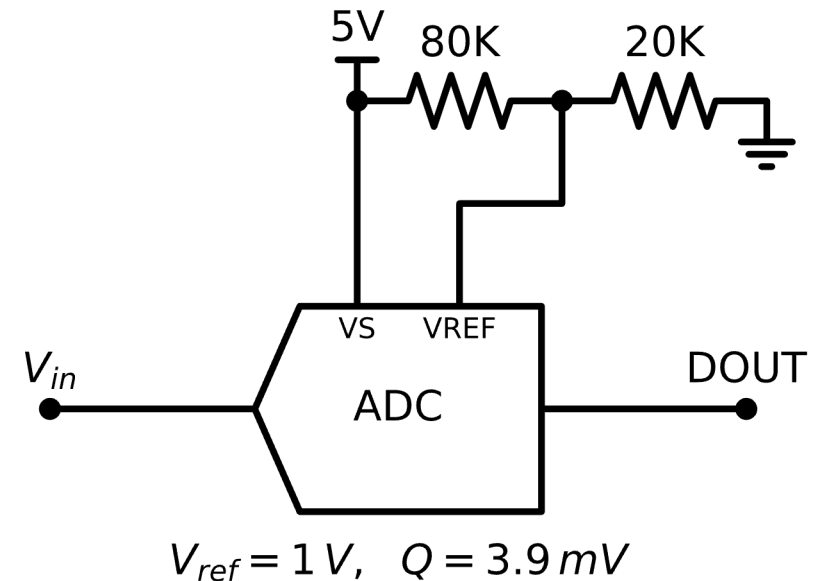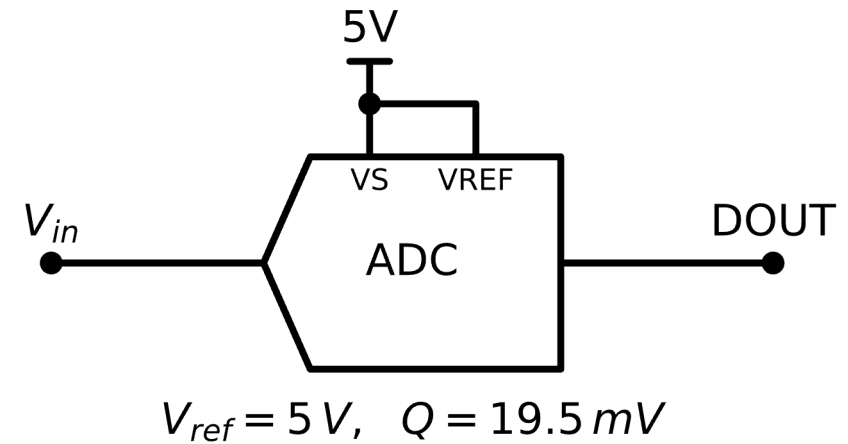How can I measure a signal in [4,5] Volts with resolution 3.9mV?



Differential ADC


- Measures the voltage difference between two input signals ($V_A - V_B$)
 - A differential voltage can be positive or negative depending which signal is higher
 - Better at rejecting noise
- The reference voltage (V_{ref}) defines the maximum value that can be measured
 - V_{ref} can be equal to the supply voltage or less
 - Voltages in $[-V_{ref}, V_{ref}]$ are linearly mapped in $[-2^{M-1}, 2^{M-1}-1]$
 - If $|V_P - V_N| > V_{ref}$, $DOUT = 2^{M-1}$ (saturation)
 - The resolution = $Q = V_{ref} / 2^{M-1}$
- Examples:
 - A 12-bit ADC with $V_{ref} = 5V$ will map:
 - $V_A = 0V$ and $V_B = 5V$ to -2048
 - $V_A = 5V$ and $V_B = 0V$ to 2047
 - $V_A = 5V$ and $V_B = 5V$ to 0
 - $V_A = 3V$ and $V_B = 2V$ to 410



$$DOUT = \frac{V_A - V_B}{V_{ref}} \cdot 2^{M-1}$$


ADC: Removing a DC Offset

- Measure a small single-ended signal with a large DC-offset
- Assuming an 8-bit ADC and supply voltage 5V
- I want to measure a signal in [4, 5] Volts with 3.9mV resolution
- Apply to the negative input a fixed 4.5V signal using a voltage divider
 - The differential signal ($V_{DIFF} = V_{in} - 4.5V$) is in [-0.5, 0.5] Volts
- With $V_{ref} = 0.5V$, I can measure the differential signal with $Q = V_{ref}/128 = 3.9 \text{ mV}$ resolution

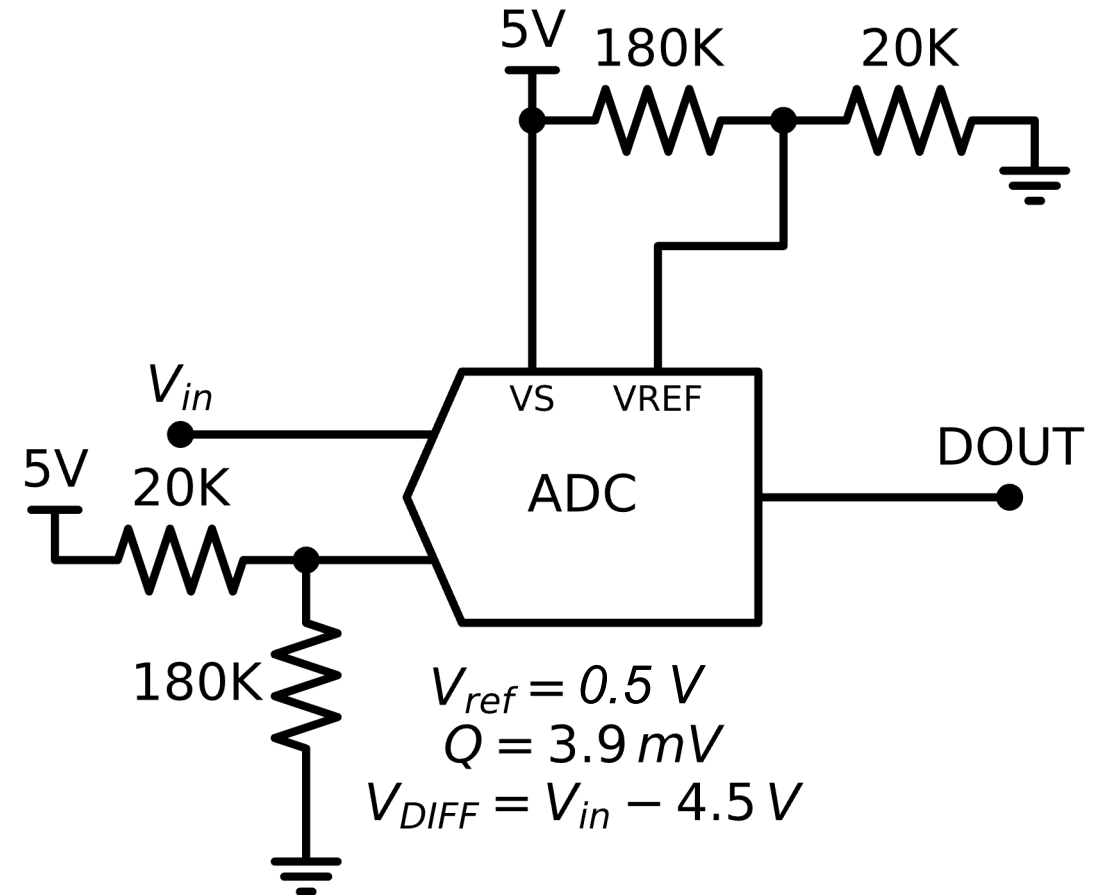

ADC Channels

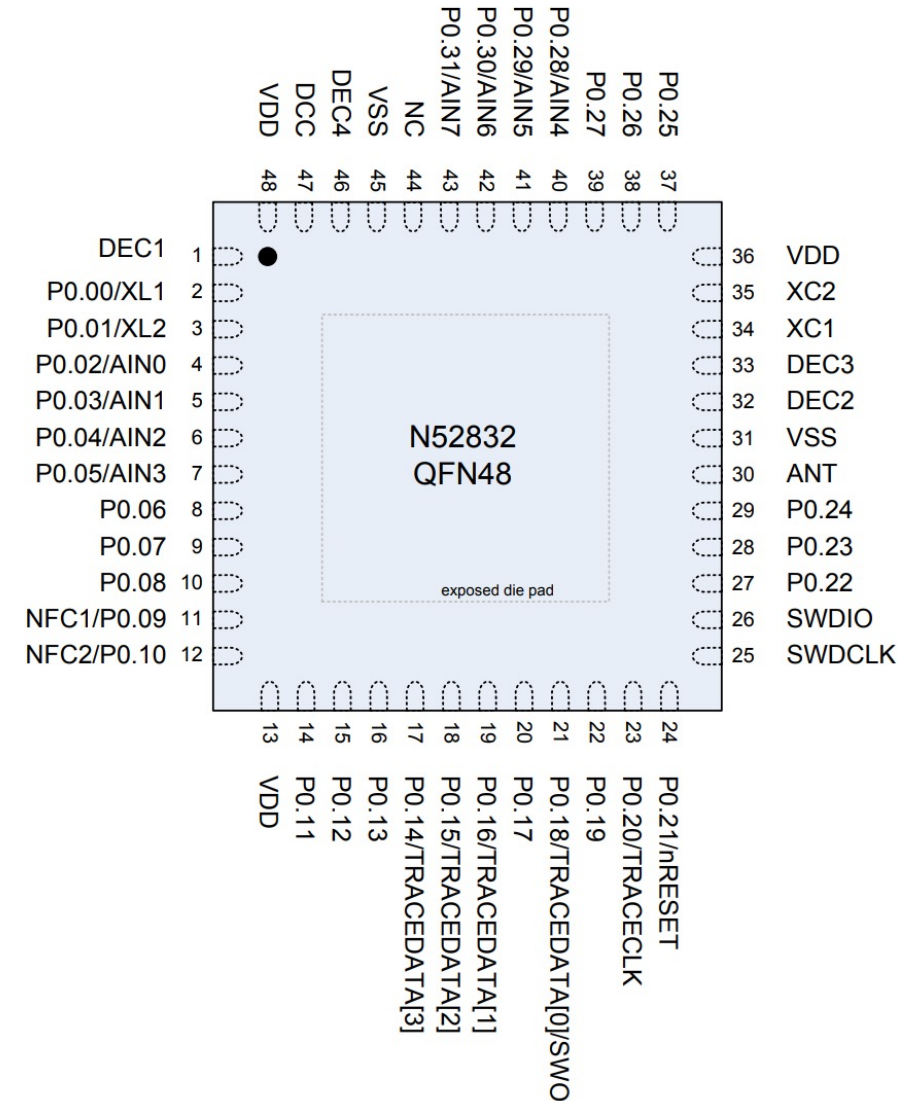- MCUs typically have internal ADCs
- Typically, the input(s) of the ADC can be internally connected to multiple external pins
- Example: the nRF2832 has 8 input channels
 - Labelled as AIN0-AIN7 in the figure
- Only one channel can be used at a time




ADC Modes of operation

- **One-shot mode:** a single sample is taken
- **Continuous mode:** samples are taken at a specified sampling frequency
 - Nyquist Theorem: to accurately represent a signal the sampling frequency should be double the highest frequency component of the input signal
- **Oversampling mode:** samples are taken at a higher than Nyquist frequency and then averaged out to reduce noise
- **Scan mode:** cycles through multiple input channels to measure multiple inputs in “parallel”


Digital-to-Analog Converter (DAC)

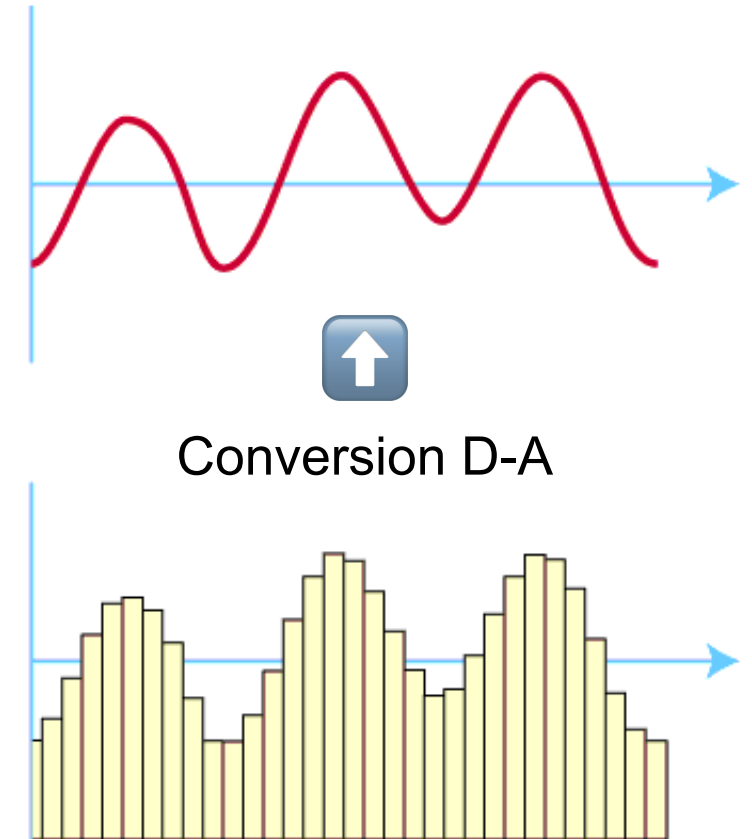- A DAC converts a digital signal (series of numbers) into an analogue signal (voltage signal)
- An DAC essentially continuous signal out of discrete time data
- Applications
 - Audio
 - Video
 - Communications (wireless/optical)
 - Digitally-controlled potentiometer
 - ...




Power Control

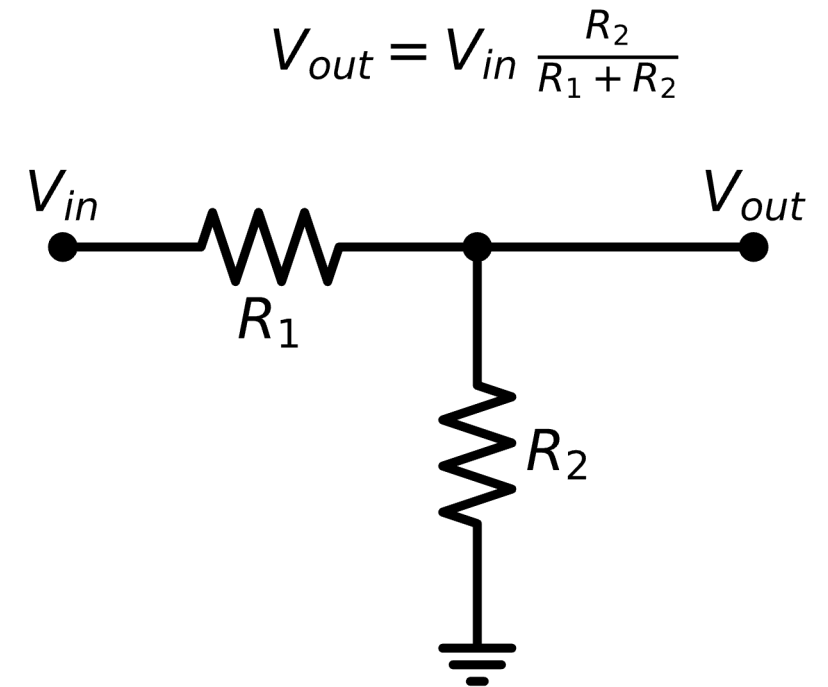- Imagine R_2 is the load
- Imagine R_1 is a variable resistor that we use to control the power that goes to the load
- If $R_1 \ll R_2$, R_1 voltage drop negligible, power consumption of R_1 also negligible
- If $R_1 \gg R_2$, R_1 current negligible, power consumption of R_1 also negligible
- If $R_1 = R_2$, R_1 consumes as much as power as the load




Dimming a LED

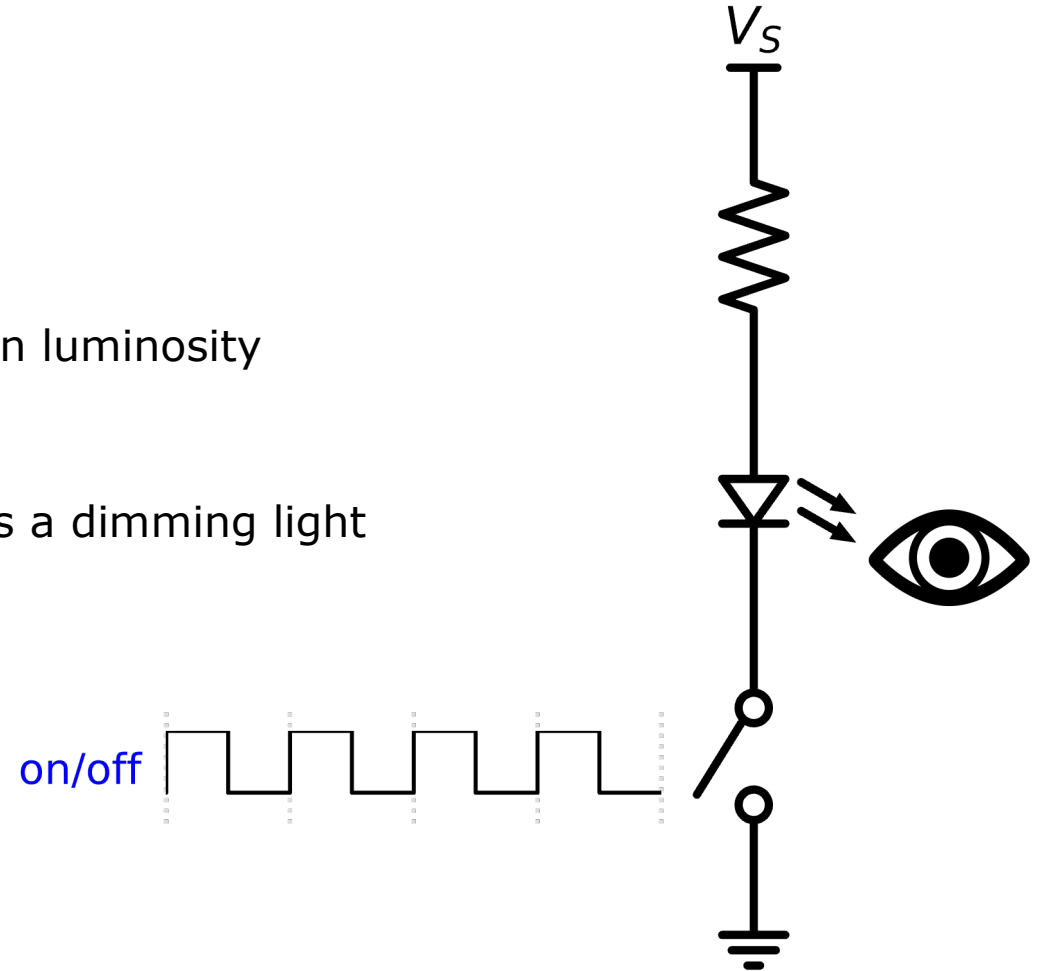- Turn LED on/off at a high frequency
- Human eye is not able to capture frequent changes in luminosity
 - Has inertia or short-term memory
- Instead, it averages out the luminosity and perceives a dimming light
 - This is a low pass filter!



Pulse Width Modulation (PWM)

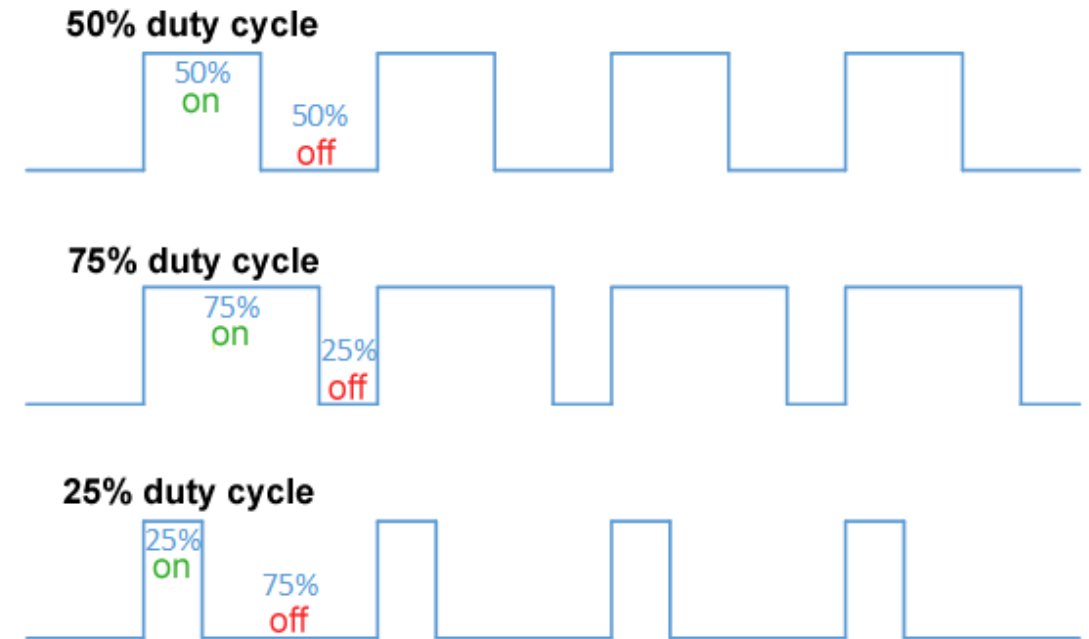- An on/off signal with two properties
 - Frequency: repetitions per second
 - Duty cycle: on time over period
- MCUs can generate PWM signals using the GPIOs



PWM Motor Control

- The PWM duty cycle controls the power that goes to the motor
- Motors are inductive
 - They react slowly on changes in current
 - Current (and thus power) through is averaged out
- Why not power control with variable series resistor (transistor)?
 - Inefficient as resistor would consume energy
 - Less power would go to the motor
 - It is easier/cheaper to generate digital signals (PWM) than analogue signals

